

Introduction to FPGA Design for Embedded Systems

Week 1 Assignment


CLASSMATE

Date :

Page :

Name - Gopalchetty Tejaswi

 Q1) Let $A = (A_1, A_0)$ and $B = (B_1, B_0)$ be the 2 numbers added, along with C_{in} as the input carry. Correspondingly, $S = (S_1, S_0)$ will be the sum and C_{out} the carry. The schematic can be hierarchially implemented by cascading 2 one-bit full adders, as shown.



1 bit full adder

The cascading is done by giving the output carry of LSB to the input carry of the MSB (as the carry done in basic addition).

$$\text{Here, } S_0 = A_0 \oplus B_0 \oplus C_{in} = A_0 \text{ XOR } B_0 \text{ XOR } C_{in}$$

$$C_1 = (A_0 \oplus B_0) \cdot C_{in} + A_0 \cdot B_0$$

$$S_1 = A_1 \oplus B_1 \oplus C_1$$


$$C_{out} = (A_1 \oplus B_1) \cdot C_1 + A_1 \cdot B_1$$

2) Let $F = A\bar{B} + C\bar{D}$

We have 2 AND arrays and 1 OR array.

So the AND arrays can be used to generate $A\bar{B}$ and $C\bar{D}$ respectively, and then these two can be added using the OR array.

Schematic:

 

LUT: $F = 1$ when $A=1, B=0$ or $C=1, D=0$

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0