

FPGA Design for Embedded Systems

Hardware Description Languages for Logic Design

An Introduction to VHDL

VHDL is a powerful and efficient language for logic design.

Now that the basics have been introduced, in this Module we will further explore how to use VHDL to design circuits through many examples and techniques.

circuits through many
examples and techniques.



University of Colorado
Boulder

Copyright © 2019 University of Colorado



Learning to Speak VHDL

Like learning any other language...

- Learn key phrases, practice them
✓ begun
- Learn Grammar and Syntax
✓ done
- Make compound sentences
- Practice, Practice, Practice

You learn grammar and
syntax, that you've done,

Writing VHDL : A 4-bit Register

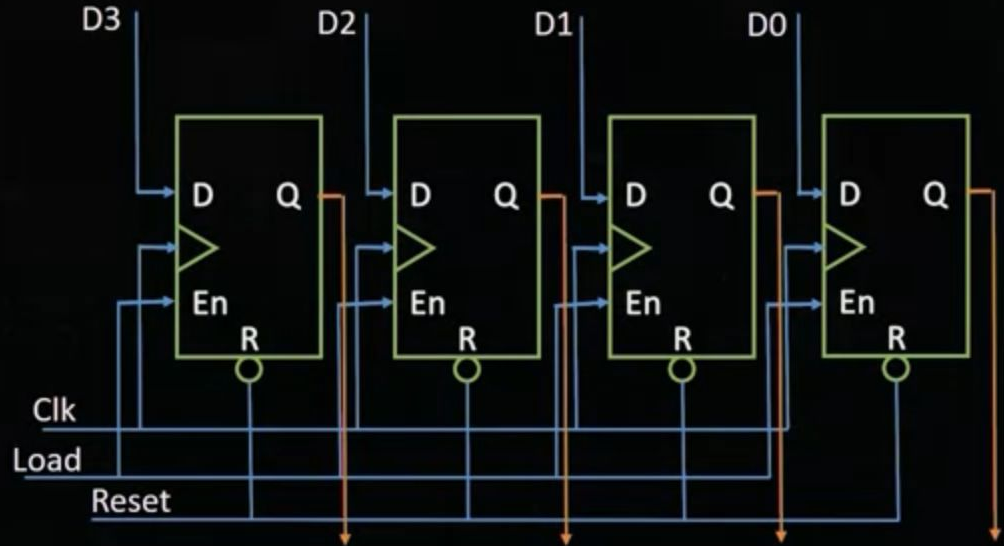 

write the VHDL to
create this circuit?


Writing VHDL : A 4-bit Register

```
-- Architecture
architecture Reg_Arch of Data_Reg is
begin dreg_proc : process (clk, reset, load)
begin
    if (reset='0') then q <= "0000";
    elsif (rising_edge(clk)) then
        if (load='1') then q <= d;
        end if;
    end if;
end process dreg_proc;
end architecture Reg_Arch;
```

If asynchronous reset then

Q output gets four zeros,

Videos in this VHDL Module

 

1. Learning to Speak VHDL (this video)
2. Combinatorial Circuits
3. Synchronous Logic: Latches and Flip Flops
4. Synchronous Logic: Counters and Registers
5. Interface: Buses and Tri-state Buffers
6. Modular Design in VHDL
7. Test Benches in VHDL - Combinatorial
8. Test Benches in VHDL - Synchronous
9. Memories in VHDL
10. Finite State Machines in VHDL

and flip flops,
counters and registers, Copyright © 2019 University of Colorado

FPGA Design for Embedded Systems

Hardware Description Languages for Logic Design

Hello and welcome to FPGA
design for embedded systems.



Combinatorial Circuits in VHDL



In this video you will learn :

- How to describe combinatorial circuits in VHDL
- How to reduce vector sizes using reduction operators

and how to reduce vector sizes
using reduction operators.



Basic Gate Assignments in VHDL

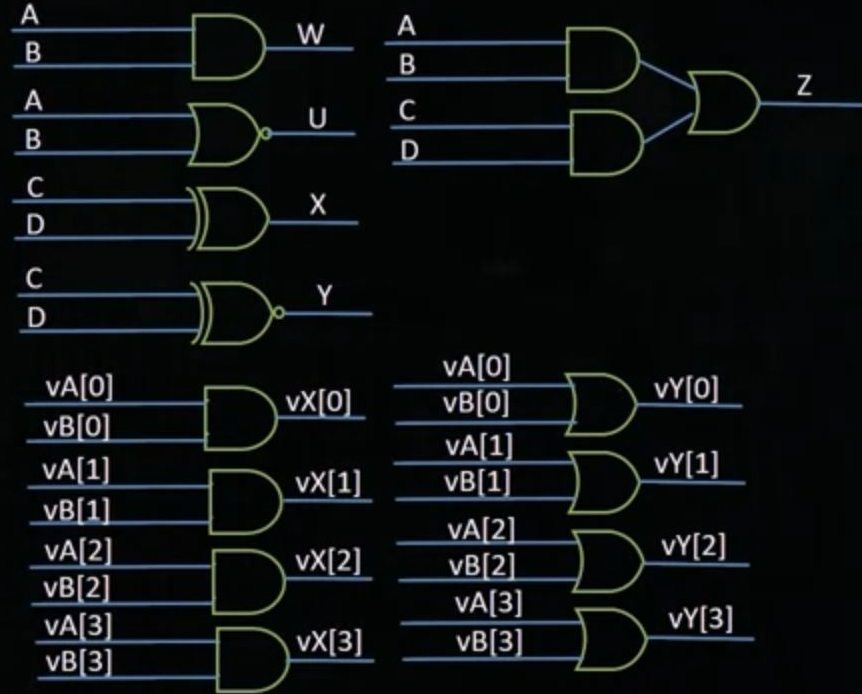 

Here we have a set of
gates: AND gates, OR gates,

Basic Gate Assignments in VHDL

```
-- Entity
entity gates is port (
    vA, vB      : in  std_logic_vector(3 downto 0);
    A,B,C,D     : in  std_logic;
    W,U,X,Y,Z   : out std_logic;
    vX, vY      : out std_logic_vector(3 downto 0)
);
end entity gates;
-- Architecture
architecture RTL of gates is
begin
    W <= A and B;      U <= A nor B;  --AND, NOR
    X <= C xor D;      Y <= C xnor D; --XOR, XNOR
    Z <= (A and B) or (C and D);      --AND-OR
    vX <= vA and vB;    -- Vector bitwise AND
    vY <= vA or vB;     -- Vector bitwise OR
end architecture RTL;
```

For VY, we have vector A
OR ed bitwise with vector B.

Vector Reduction in VHDL

```
-- Entity : Note: use IEEE.std_logic_misc.all;
entity gates is port (
    vA, vB, vC, vD : in  std_logic_vector(3 downto 0);
    W,U,X,Y,Z      : out std_logic );
end entity gates;

-- Architecture : reduction after VHDL-2008 tools
architecture RTL of gates is
begin
    W <= AND_REDUCE(vA); -- Vector Reduction AND
    U <= NOR_REDUCE(vB); -- Vector Reduction NOR
    X <= XOR_REDUCE(vD); -- Vector Reduction XOR
    Y <= OR_REDUCE(vA) and vB(0); -- OR Red, bit AND
    Z <= OR_REDUCE(vA and vB);    -- Bit AND, OR Red
end architecture RTL;
```

we have a built in function
in the VHDL library.

In VHDL, you can use either of the following as an XOR reduction for bus A = "1011" :

a) `z_out <= XOR (A);`

b) `z_out <= XOR_REDUCE(A);`



☒ TRUE.

Correct

Yes, using VHDL-2008 XOR reduces just like the function XOR_REDUCE.

☐ FALSE.

Vector Reduction in VHDL

  

So we have vector A
bitwise AND ed for W,


Procedural Logic in VHDL

```
-- Entity
entity gates is port (
    A,B,C,D      : in  std_logic;
    Y             : out std_logic );
end entity gates;

-- Architecture
architecture combo of gates is
begin combo_process : process (A,B,C,D)
begin
    if      ((C='1') and (D='1')) then Y <= '0';
    elsif  ((A='1') or  (B='1')) then Y <= '1';
    else    Y <= '0';
    end if;
end process combo_process;
end architecture combo;
```

we can create a statement with

Procedural Logic in VHDL - Circuit

 

we have A OR-ed with B,





Procedural Logic – Gotcha, Latch Generate

```
-- Entity
entity gates is port (
  A,B,C,D      : in  std_logic;
  Y             : out std_logic   );
end entity gates;

-- Architecture
architecture combo of gates is
begin combo_process : process (A,B,C,D)
begin
  if      ((C='1') and (D='1')) then Y <= '0';
  elsif  ((A='1') or  (B='1')) then Y <= '1';
  end if;  -- Missing Else condition for Y
end process combo_process;
end architecture combo;
```

missing which zeroed out the Y,

  Procedural Logic – Gotcha, Latch Generate Incomplete Assignment



So in the same case,

Summary – VHDL for Combinatorial Circuits

In this video, you have learned:

- How to describe combinatorial circuits in VHDL using either assignment statements
- How to reduce vector sizes using operators as bus to bit reduction operators
- How to prevent unintentional latches in logic circuits

using assignment statements,


FPGA Design for Embedded Systems

Hardware Description Languages for Logic Design

Hello, and welcome back to

Synchronous Logic : D Latch

How can we make a D Latch in VHDL?

 

synchronous logic as well
as combinatorial logic.



University of Colorado
Boulder

Copyright © 2019 University of Colorado

Synchronous Logic : D Latch

```
-- Entity
entity DLatches is port (
    d, gate, clr      : in  std_logic;
    q                  : out std_logic );
end entity DLatches;
-- Architecture
architecture LArch of DLatches is begin
    latch_proc_1 : process (gate, d)
    begin
        if      (gate='1') then q <= d;
            -- No rising_edge()

        end if;
        -- No gate=0 value, so latch inferred
    end process latch_proc_1;
```

In this case, we have a
process sensitivity with GATE,



Synchronous Logic : D Latch

-- another Latch example

```
latch_proc_2 : process (gate, d, clr)
begin
    if    (clr ='1') then  q <= '0';
    elsif (gate='1') then  q <= d;
    end if;
end process latch_proc_2;
end architecture LArch;
```

d and clear as an input.



Combinatorial Logic


- Finite time for best case or worst case logic value to propagate a result through wires and logic cells across the chip
- 0 → 1 transition for path C to Y
 - $0.2 + 0.9 + 0.3 + 1.1 + 0.2 = 2.7$ nano seconds



Combinatorial logic is END gates,

Synchronous Logic


- Logic path synchronized to CLK

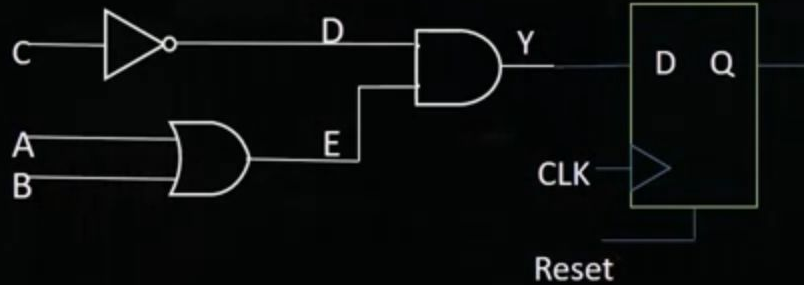

If we wanted to
synchronize this path,

Synchronous Logic : D Flip Flop

How can we make a D Flip Flop in VHDL?

 

D input, clock trigger,

Synchronous Logic : D Flip Flop – Sync Reset

```
-- Entity
entity DFF is port (
    d, clk, reset      : in  std_logic;
    q                  : out std_logic );
end entity DFF;
```

and a q as an output.

Synchronous Logic : D Flip Flop – Sync Reset

```
-- Architecture,  
-- could use (clk'event and clk='1')  
architecture DFF_Arch of DFF is  
begin dff_proc_1 : process (clk)  
begin  
    if (rising_edge(clk)) then  
        if (reset='1') then q <= '0';  
            -- Sync Reset  
        else q <= d;  
        end if;  
    end if;  
end process dff_proc_1;  
end architecture DFF_Arch;
```

In this case, we could
also use clock tick

Either of the following constructs will create a Flip-Flop :

a) if (clk'event and clk='1') then

b) if (rising_edge(clk)) then

☒ True.

Correct

Right. Either method will create a Flip-Flop.

☐ False.

Synchronous Logic : D Flip Flop – Async Reset



```
-- Entity
entity DFF is port (
    d, clk, set, reset    : in  std_logic;
    q                     : out std_logic );
end entity DFF;
-- Architecture, next slide
```

Our entity looks
similar d clock set,



Synchronous Logic : D Flip Flop – Async Reset

How can we make a D Flip Flop in VHDL?

  

create a D flip flop with
an asynchronous reset?



Synchronous Logic : D Flip Flop – Async Reset

```
-- Architecture
architecture DFF_Arch of DFF is
begin dff_proc_2 : process (clk, set, reset)
begin
    if      (reset='1')           then q <= '0';
        -- Async
    elsif (rising_edge(clk)) then
        if      (set='0')           then q <= '1';
            -- Sync
        else
            q <= d;
            -- Sync
        end if;
    end if;
end process dff_proc_2;
end architecture DFF_Arch;
```

and here's our architecture.

Synchronous Logic : D Flip Flop

How can we make a Clock Enable in VHDL?

  

How would we make a d flip
flop with a clock enable? Copyright © 2019 University of Colorado

Synchronous Logic : D Flip Flop – Clock Enable

```
-- Entity
entity DFF is port (
    d, clk, ce, reset    : in  std_logic;
    q                    : out std_logic );
end entity DFF;
-- Architecture Next Slide
```

Similar entity, d clock,

Synchronous Logic : D Flip Flop – Clock Enable

```
-- Architecture
architecture DFF_Arch of DFF is
begin dff_proc_3 : process (clk, ce, reset)
begin
    if      (reset='1')           then  q <= '0';
        -- Async
    elsif (rising_edge(clk)) then
        if      (ce='1')           then  q <=  d;
            -- Sync
        end if;
    end if;
end process dff_proc_3;
end architecture DFF_Arch;
```


Here's our architecture for



Summary – VHDL for Synchronous Circuits

In this video, you have learned:

 - How to describe synchronous circuits in VHDL
- How to design flip flops with synchronous and asynchronous set and reset



In this video, you've
learned how to